



UStomp.com - Ibanez TS-808 It's the tube screamer. Considered by many to be the overdrive pedal.

the overdrive pedal.

Transistors should be low noise NPN 2N5088 or 2N3904 IC should be a 4558

Diodes should be 1N914's

Layout and presentation © 2003 Steven Rittmeyer.
All rights reserved. Authorization for personal use only.
Any commercial use is forbidden.
Permission for posting/serving limited to http://www.ustomp.com
Permission refused for serving from or posting to other sites.